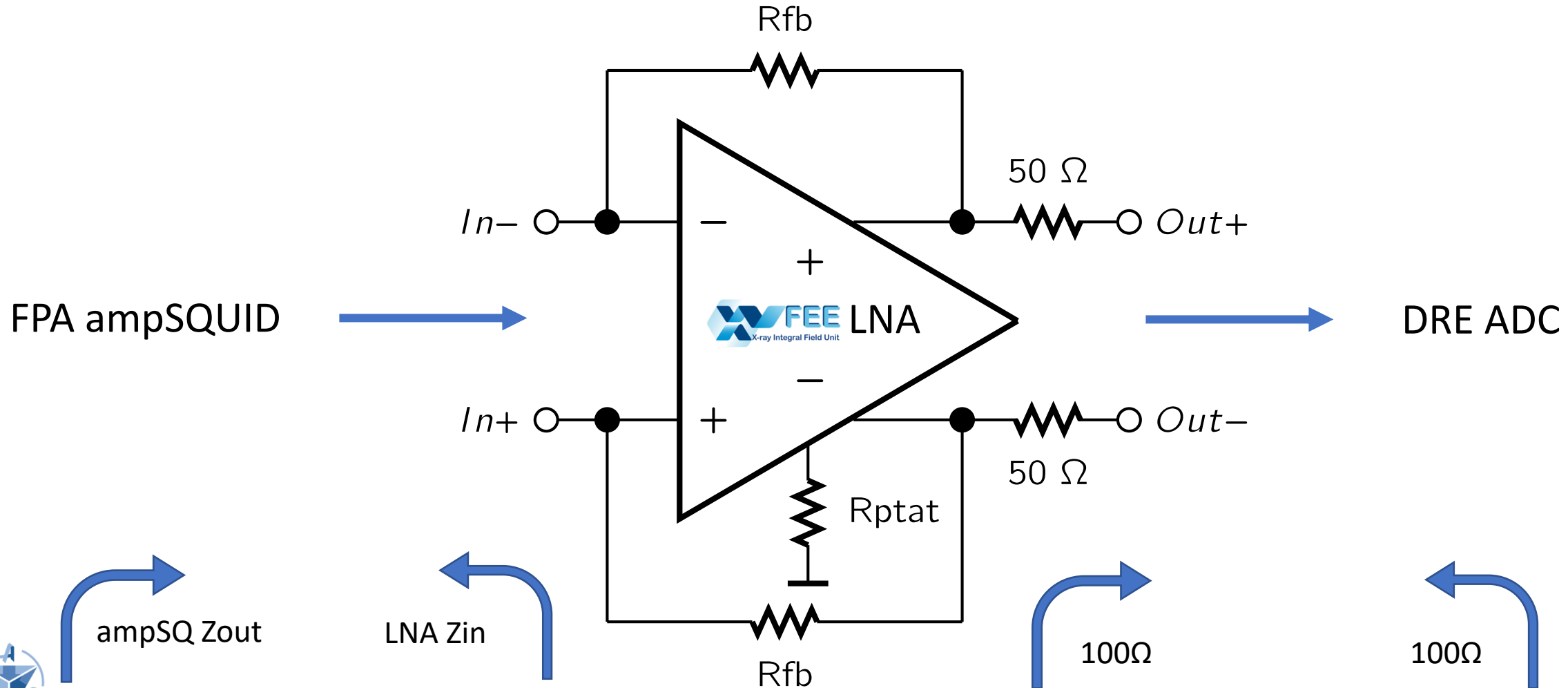



LNA input impedance matching & noise reduction

X-IFU CM#13 – Technical Session - Mai 2022 – Damien Prêle for the APC WFEE team



Miller effect -> LNA $Z_{in} \sim R_{fb}/(1-LNA_Gain)$

R_{dyn} in small signal
 R_{dc} in DC

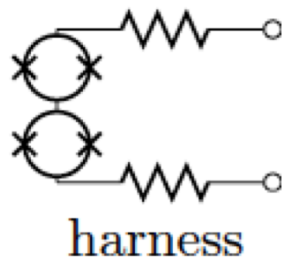


The feedback “subtract”
 an **half of the input signal**
 and an **half of the noise !**
 Even the intrinsic LNA Noise

$R_{dyn} + \text{harness} = LNA\ Z_{in}$

0.5 V/V



ampSQ Z_{out}
 + harness resistances

$\sim R_{fb}/(1-|LNAgain|)$

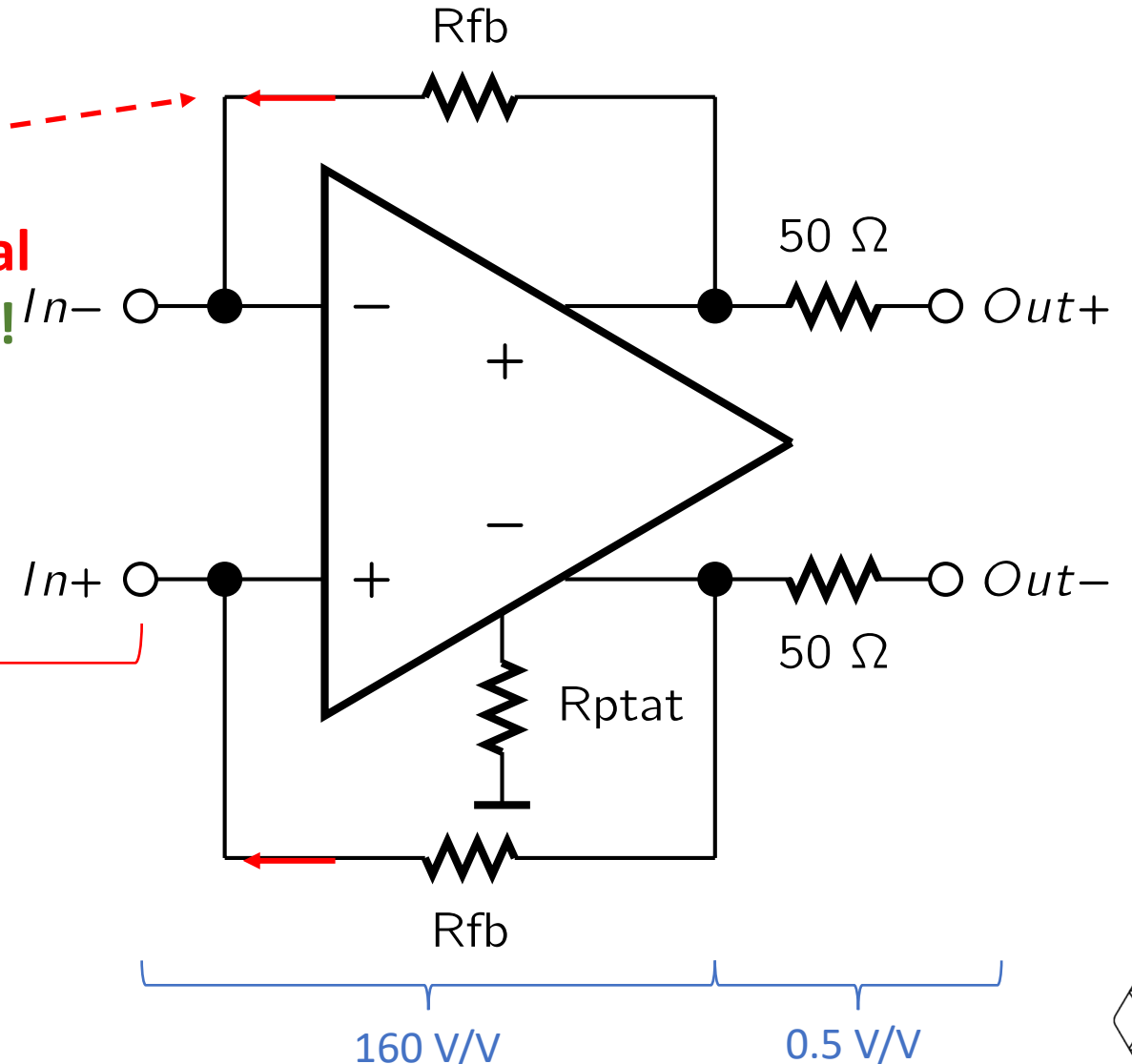

LNA noise subtraction

LNA noise (as signal) is “subtract”

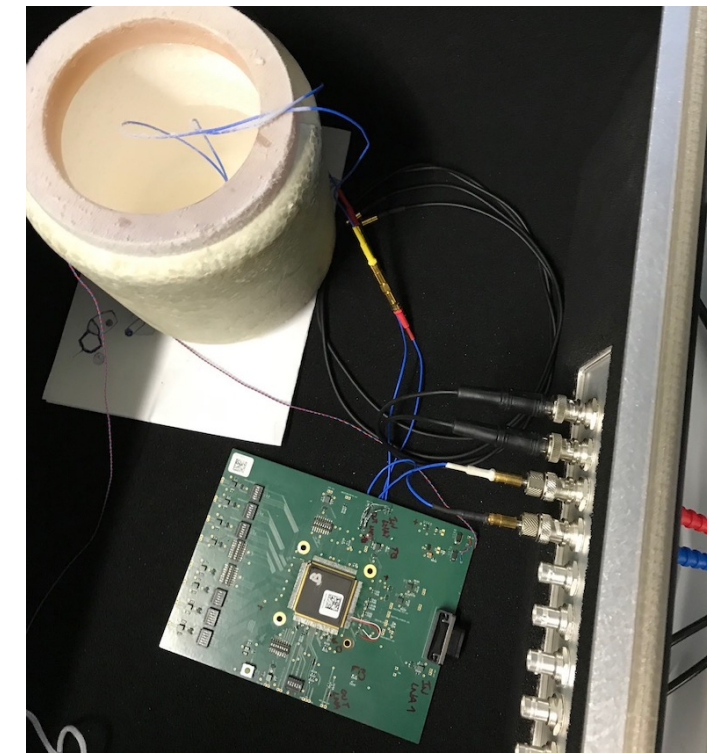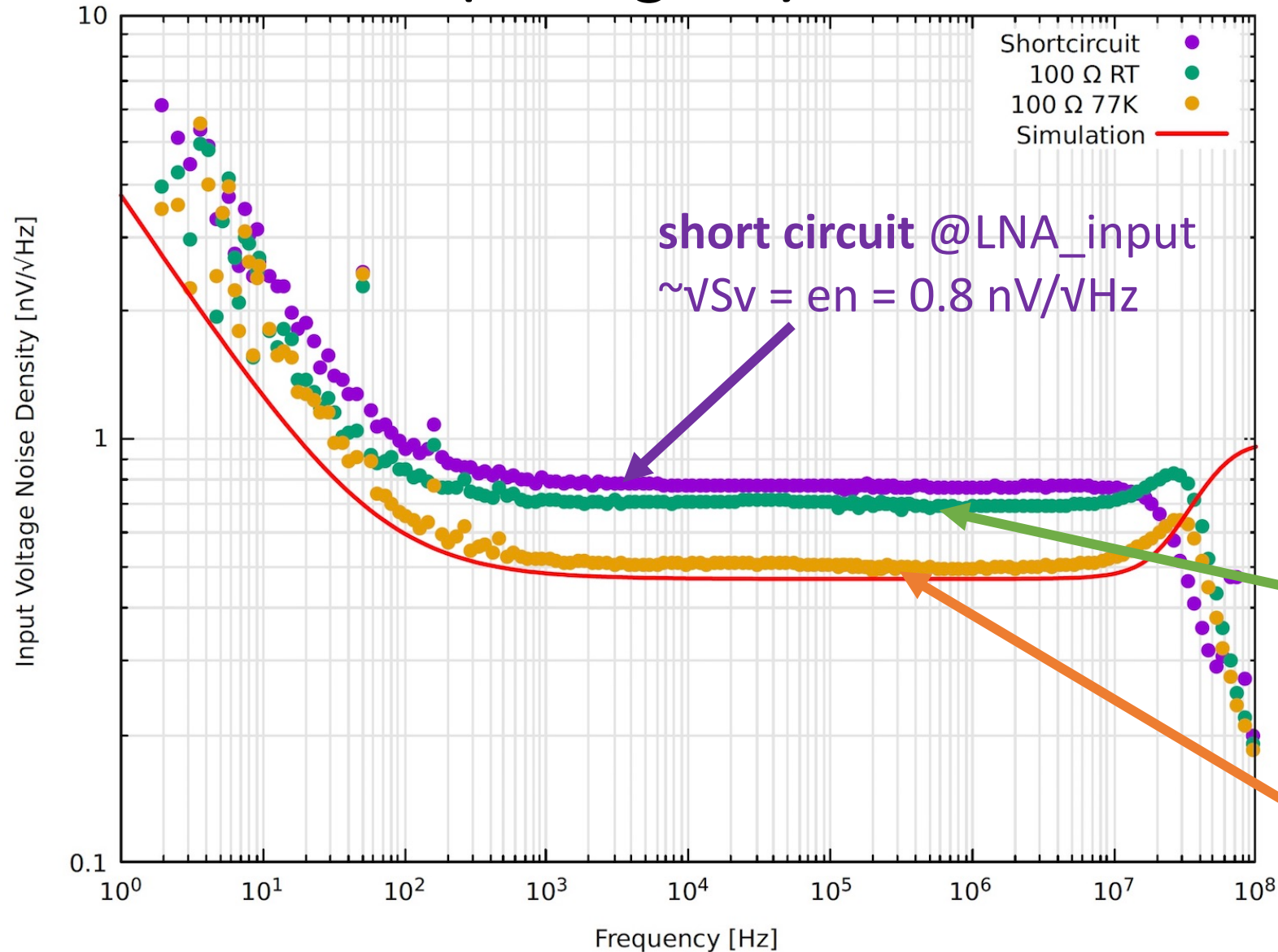

T=300K 100Ω @LNA input

$$S_v = (e_n/2)^2 + (1.3 \text{ nV}/\sqrt{\text{Hz}}/2)^2$$


$$\sqrt{S_v} = 0.75 \text{ nV}/\sqrt{\text{Hz}}$$

T=77K 100Ω @LNA input

$$S_v = (e_n/2)^2 + (0.65 \text{ nV}/\sqrt{\text{Hz}}/2)^2$$

$$\sqrt{S_v} = 0.5 \text{ nV}/\sqrt{\text{Hz}}$$

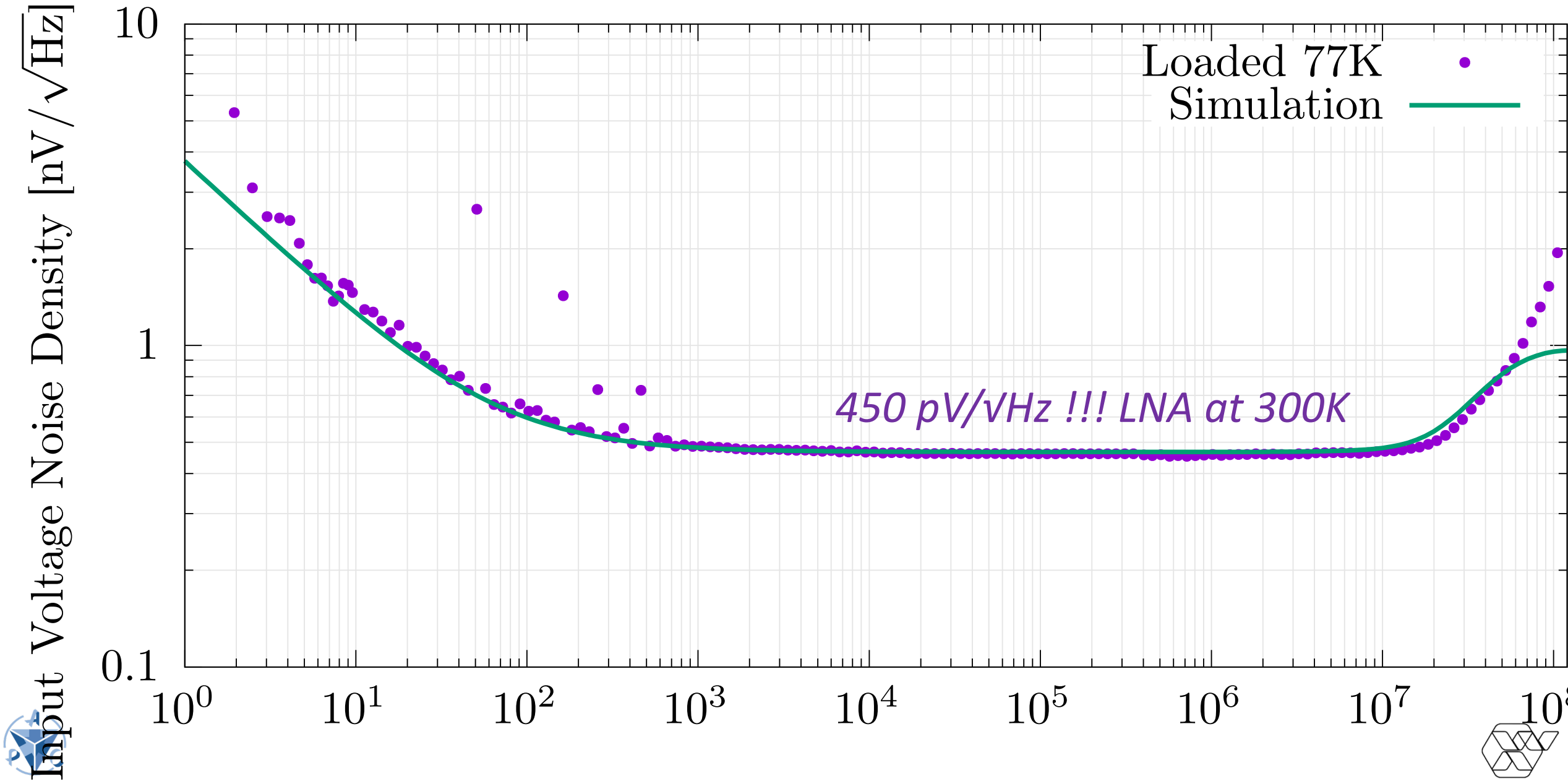One of the last measured LNA noise (with gain(f) correction)



LNA Z_{in}

$I_b \sim 10 \mu A$

$4 mA$





R_{fb}

$$+ \text{in} // \text{Rfb}/(1-\text{LNAGain})$$

The diagram illustrates a fully differential amplifier (FDA) configured as a differential-to-single-ended converter. The circuit includes an FDA with inputs $In+$ and $In-$ and outputs $Out+$ and $Out-$. The inputs are biased with current sources I_b . The feedback network consists of a resistor R_{fb} connected between the outputs and a resistor R_{ptat} connected from the output $Out-$ to ground. The output $Out+$ is connected to a $50\ \Omega$ load resistor. The feedback resistor R_{fb} is labeled with a value of $\sim 90\text{mV}$. The overall gain is indicated as 160 V/V , and the output impedance is 0.5 V/V .

LNA

Gain, Phase and Zin measurement

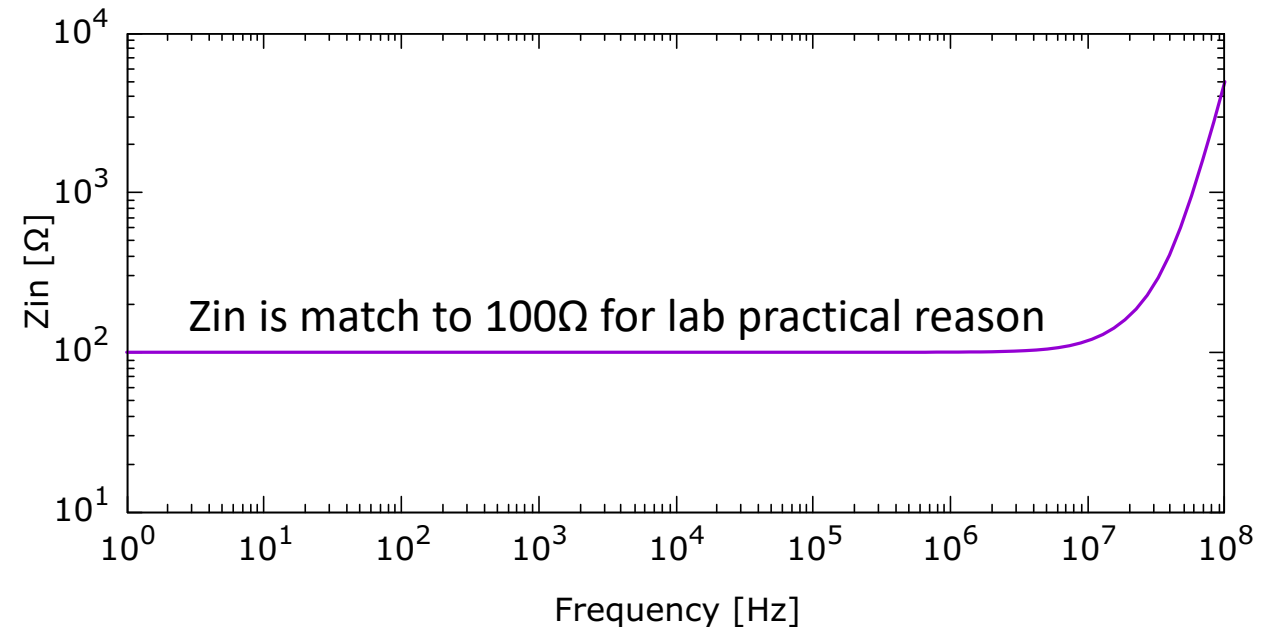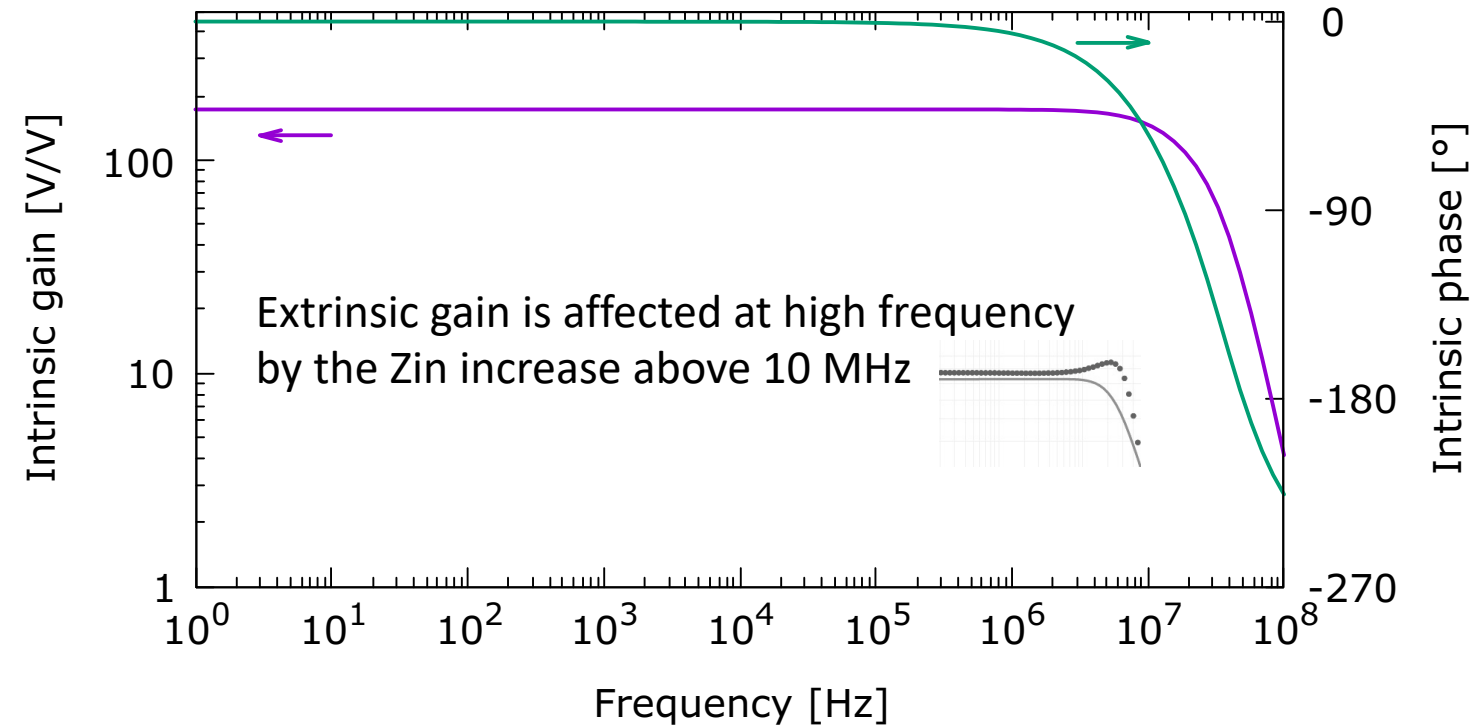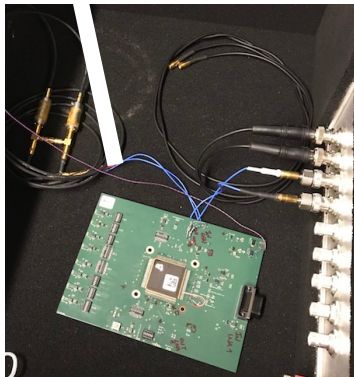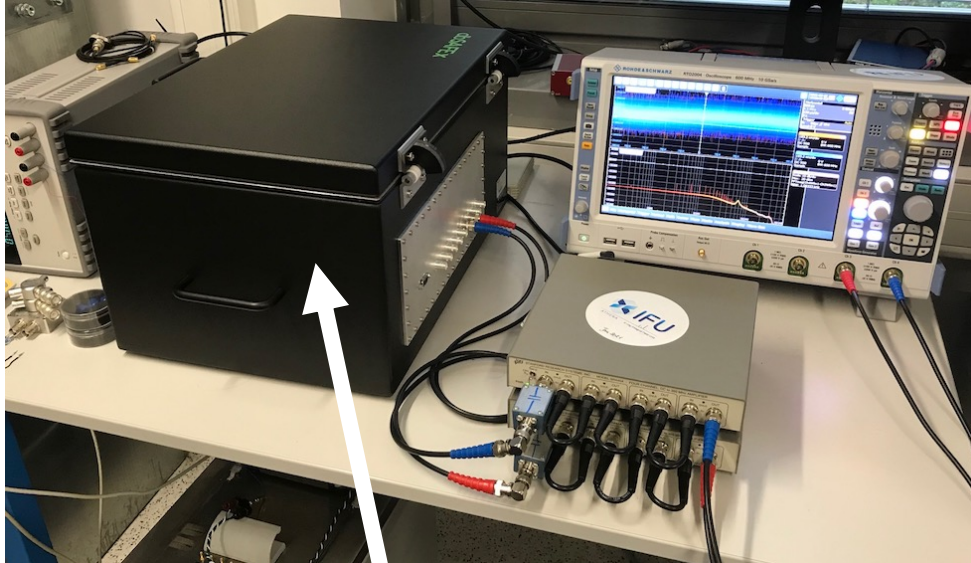

More details about ampSQUID Zout ?



Using ATHENA SQUID TN5.1 Test Report FAB1 (ATH-SQ-VTT-TN-5.1) 27.03.2020


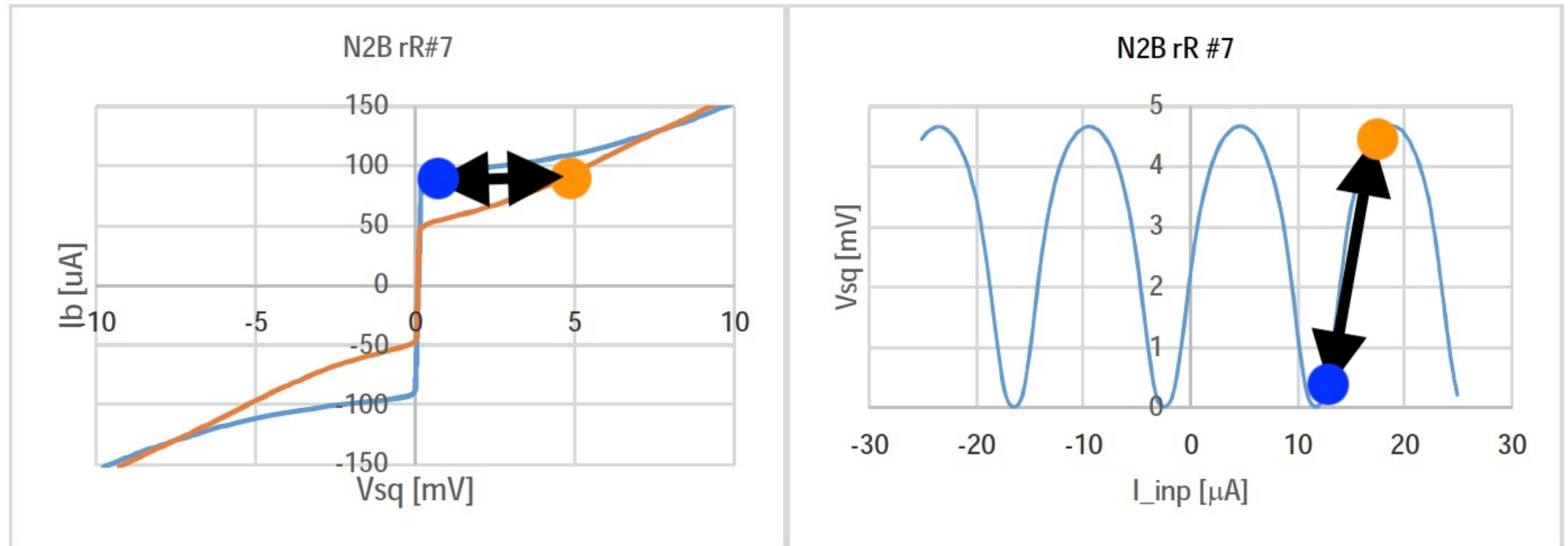


Fig. 7: Voltage-current characteristics and flux response of a N2B-type booster SQUID at $T = 4.2$ K. The device has close-to nominal upper critical current in the IV characteristics.


More details about ampSQUID Zout

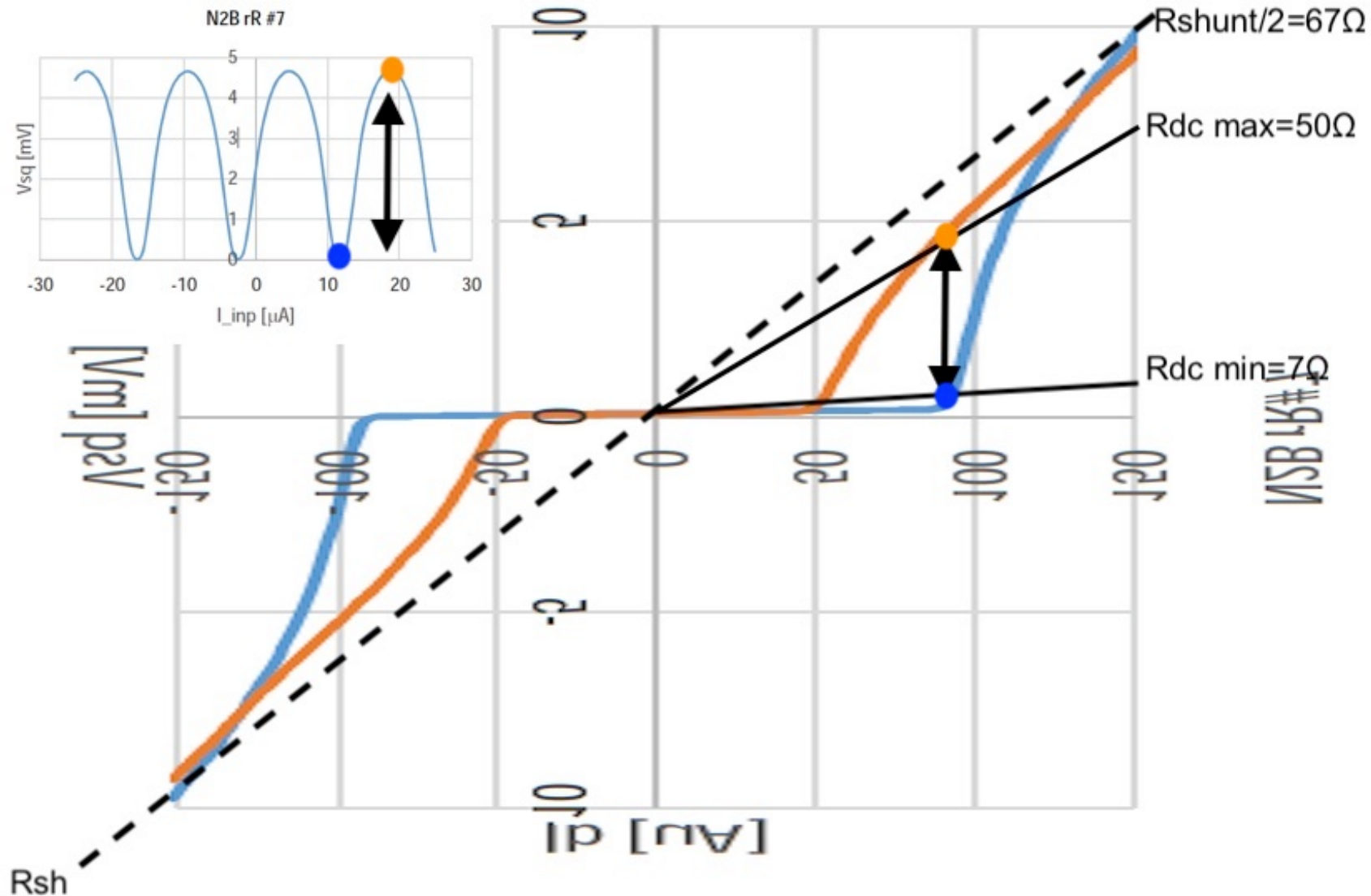SQUID output charac $V(I)$
 $\rightarrow V/I = R_{dc}$ [7Ω-50Ω]




More details about ampSQUID Zout

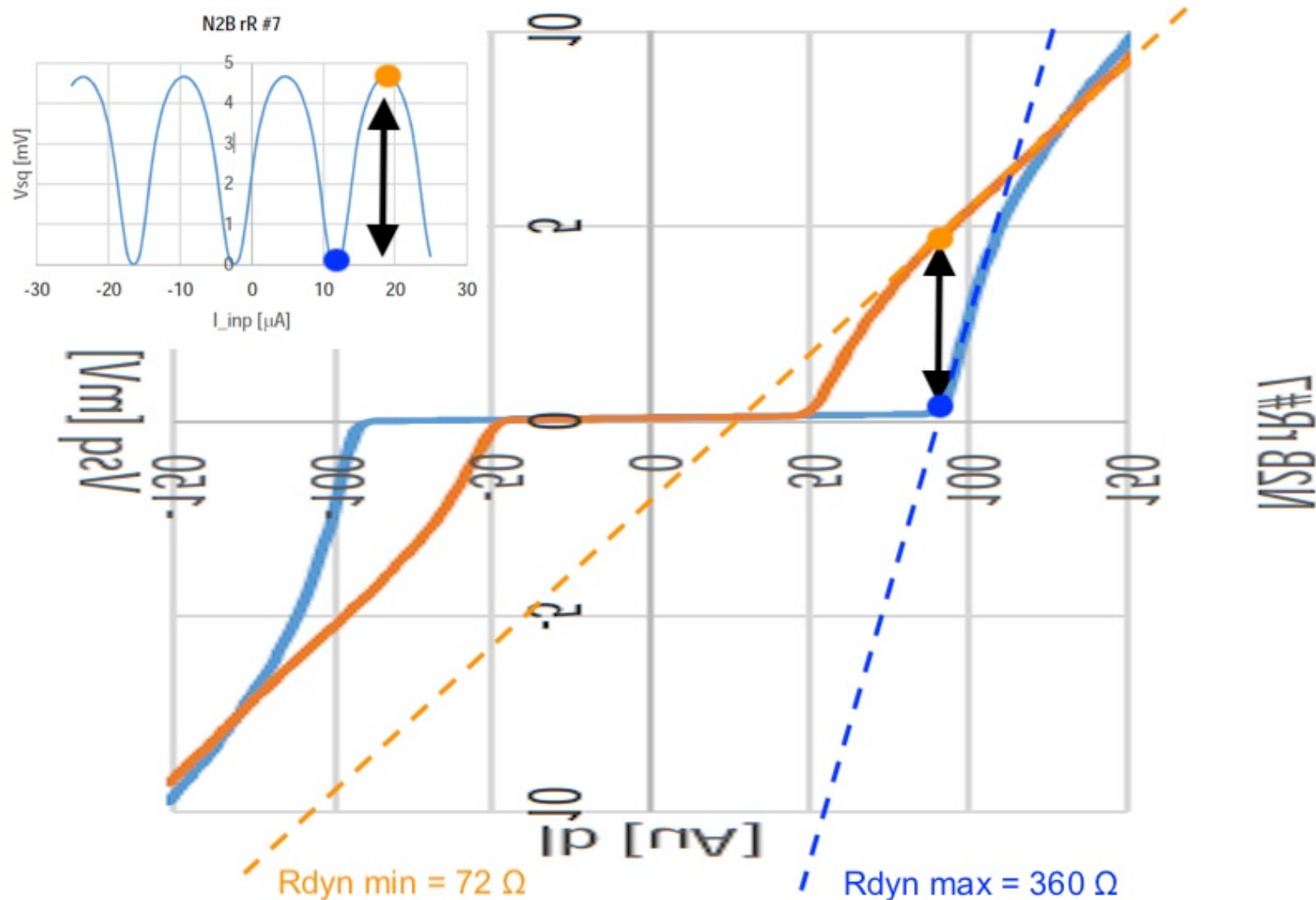SQUID output charac $V(I)$
 $\rightarrow V/I = R_{dyn} [72\Omega - 360\Omega]$



Where the SQUID biasing current will go ?

In DC
ZampSQ+Harness~**75Ω** (?)

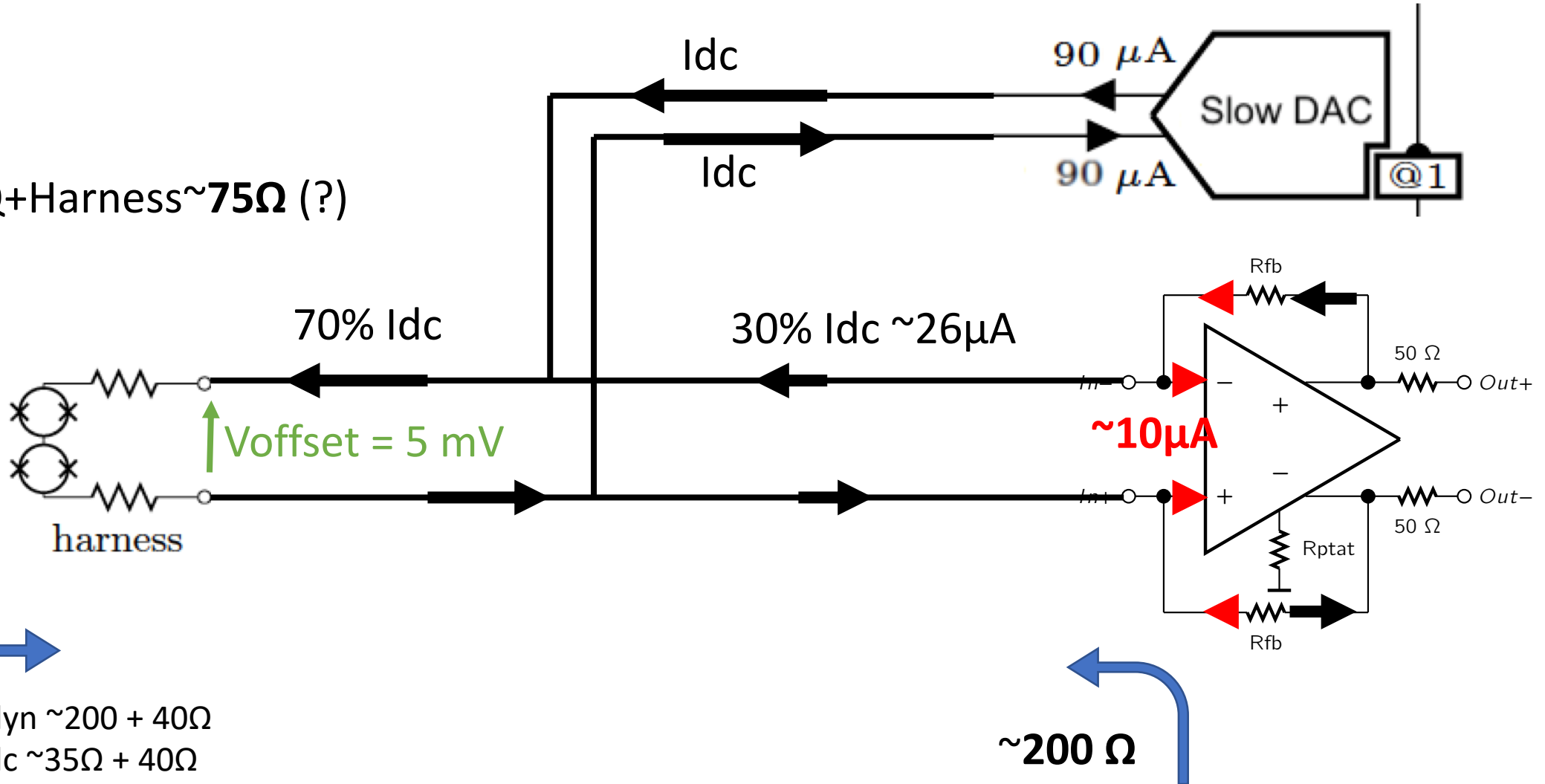

Possible use of a separate line for the bias ?

